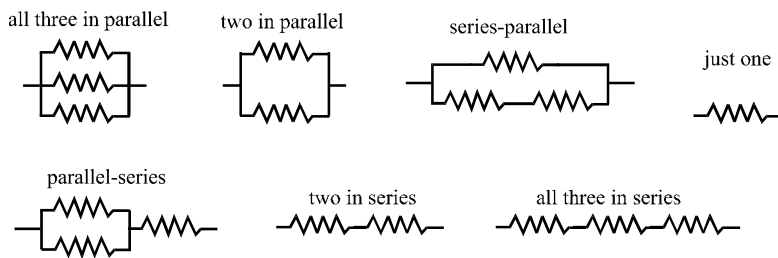


In this chapter, the following convenient calculation of equivalent resistance for two resistors in parallel is

used in many exercises. $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$, $\Rightarrow R_p = \frac{R_1 R_2}{R_1 + R_2}$.

1. (b).
2. (a).
3. (b).
4. (b).
5. (a).
6. (b).
7. **No**, not generally. However **if all resistors are equal**, the voltages across them are the same.
8. **No**, not generally. However **if all resistors are equal**, the currents through each is the same.
16. (a) You can get **(3) seven** different values of equivalent resistance.



(b) All three in parallel: $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = 3 \frac{1}{4.0 \Omega} = \frac{3}{4.0 \Omega}$, $R_p = \boxed{1.3 \Omega}$.

Two in parallel: $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = 2 \frac{1}{4.0 \Omega} = \frac{2}{4.0 \Omega}$, $R_p = \boxed{2.0 \Omega}$.

Two in series-parallel: $\frac{1}{R_p} = \frac{1}{R_s} + \frac{1}{R} = \frac{1}{R+R} + \frac{1}{R} = \frac{3}{2(4.0 \Omega)}$, $R_p = \boxed{2.7 \Omega}$.

Just one alone: $R = \boxed{4.0 \Omega}$.

Two in parallel-series: $R_s = R + R_p = R + \frac{R R}{R + R} = \frac{3R}{2} = \frac{3(4.0 \Omega)}{2} = \boxed{6.0 \Omega}$.

Two in series: $R_s = R_1 + R_2 = 4.0 \Omega + 4.0 \Omega = \boxed{8.0 \Omega}$.

All three in series: $R_s = R_1 + R_2 + R_3 = 3(4.0 \Omega) = \boxed{12 \Omega}$.

26. R_1 and R_2 are in series: $R_s = 2.0 \Omega + 2.0 \Omega = 4.0 \Omega$.

R_s , R_3 , and R_4 are in parallel: $\frac{1}{R_p} = \frac{1}{4.0 \Omega} + \frac{1}{2.0 \Omega} + \frac{1}{2.0 \Omega} = \frac{5}{4.0 \Omega}$.

27. R_2 and R_3 are in series: $R_s = 6.0 \Omega + 4.0 \Omega = 10 \Omega$.

R_s , R_1 , and R_4 are in parallel: $\frac{1}{R_p} = \frac{1}{10 \Omega} + \frac{1}{6.0 \Omega} + \frac{1}{10 \Omega} = \frac{22}{60 \Omega}$, $\Rightarrow R_p = \boxed{2.7 \Omega}$.

So $R_p = \frac{4.0 \Omega}{5} = \boxed{0.80 \Omega}$.

28. $R_2, R_3,$ and R_4 are in series: $R_s = 20 \Omega + 5.0 \Omega + 5.0 \Omega = 30 \Omega$.

R_s and R_1 are in parallel: $R_p = \frac{(30 \Omega)(10 \Omega)}{30 \Omega + 10 \Omega} = \boxed{7.5 \Omega}$.

$\boxed{36}$. (a) $I_1 = \frac{V}{R_1} = \frac{6.0 \text{ V}}{6.0 \Omega} = \boxed{1.0 \text{ A}}$ R_2 and R_3 are in series. $R_s = 4.0 \Omega + 6.0 \Omega = 10 \Omega$.

So $I_2 = I_3 = \frac{6.0 \text{ V}}{10 \Omega} = \boxed{0.60 \text{ A}}$, $I_4 = \frac{6.0 \text{ V}}{10 \Omega} = \boxed{0.60 \text{ A}}$.

(b) $P_1 = I_1^2 R_1 = (1.0 \text{ A})^2 (6.0 \Omega) = \boxed{6.0 \text{ W}}$, $P_2 = (0.60 \text{ A})^2 (4.0 \Omega) = \boxed{1.4 \text{ W}}$,

$P_3 = (0.60 \text{ A})^2 (6.0 \Omega) = \boxed{2.2 \text{ W}}$, $P_4 = (0.60 \text{ A})^2 (10 \Omega) = \boxed{3.6 \text{ W}}$.

(c) $P_{\text{sum}} = 6.0 \text{ W} + 1.44 \text{ W} + 2.16 \text{ W} + 3.6 \text{ W} = 13 \text{ W}$.

From Exercise 18.27, $P_{\text{total}} = \frac{(6.0 \text{ V})^2}{2.7 \Omega} = 13 \text{ W}$. Therefore $\boxed{P_{\text{sum}} = P_{\text{total}} = 13 \text{ W}}$.

43. (a).

44. (a).

45. (d).

46. (b).

55. Around the loop in a counterclockwise direction, $20 \text{ V} - I(20 \Omega) - 10 \text{ V} - I(10 \Omega) = 0$,

so $I = I_1 = I_2 = 0.33 \text{ A}$. Therefore $\boxed{I_1 = 0.33 \text{ A (left)}}$ and $\boxed{I_2 = 0.33 \text{ A (right)}}$.

60. (a). The voltage across the resistor decreases exponentially when a capacitor is discharged.

61. (c). The current in the circuit decreases exponentially when a capacitor is charged.

62. (c). $\tau = RC$.

63. (b). $\tau = RC$, independent of charges.

71. (a) $\tau = RC$, $R = \frac{\tau}{C} = \frac{1.50 \text{ s}}{1.00 \times 10^{-6} \text{ F}} = 1.50 \times 10^6 \Omega = \boxed{1.50 \text{ M}\Omega}$.

(b) $V_C = V_o(1 - e^{-t/\tau}) = (12.0 \text{ V})(1 - e^{-3}) = \boxed{11.4 \text{ V}}$.

76. (a).

77. (b).

78. (b).

86. An ammeter is connected in series. $I = \frac{V}{R + R_a} = \frac{6.0 \text{ V}}{10 \Omega + 1.0 \times 10^{-3} \Omega} = \boxed{0.59994 \text{ A}}$.

87. A voltmeter is connected in parallel. $I = \frac{V}{R_v} = \frac{6.0 \text{ V}}{30 \times 10^3 \Omega} = 2.0 \times 10^{-4} \text{ A} = \boxed{0.20 \text{ mA}}$.

90. (a).

91. (c).

92. $\boxed{\text{The fuse and the switch are on the ground side of the circuit}}$. An open switch or blown fuse would potentially leave the motor at a high voltage if it were touched by a person.

93. No, a high voltage can produce high harmful current, even if resistance is high, because current is caused by voltage (potential difference).

94. A conductor has very low resistance. The resistance of the wire between the feet is very small; so

the voltage between the feet is small. Therefore the current through the bird is also small.

107. (a) $V_C = V_0 e^{-t/\tau}$, $\Rightarrow 20.0 \text{ V} = (10\,000 \text{ V}) e^{-t/\tau}$.

$$e^{-t/\tau} = 0.00200 \quad \text{so} \quad \frac{t}{\tau} = 6.215. \quad \text{Therefore} \quad \tau = \frac{t}{6.215} = \frac{75.1 \times 10^{-3} \text{ s}}{6.215} = 12.08 \text{ ms} = \boxed{12.1 \text{ ms}}.$$

$$(b) \tau = RC, \quad \Rightarrow R = \frac{\tau}{C} = \frac{12.08 \times 10^{-3} \text{ s}}{10.0 \times 10^{-6} \text{ F}} = 1.208 \text{ k}\Omega = \boxed{1.21 \text{ k}\Omega}.$$

(c) Because $U_C = \frac{1}{2} CV^2$, losing 90% of its energy means the remaining energy is 10% = 0.10.

The remaining voltage is then $\sqrt{0.10} = 0.316$ (31.6%) of its maximum voltage.

$$0.316 = e^{-t/\tau}, \quad \Rightarrow \frac{t}{\tau} = -\ln(0.316) = 1.15.$$

$$\text{Therefore} \quad t = 1.15\tau = 1.15(12.08 \text{ ms}) = \boxed{13.9 \text{ ms}}.$$