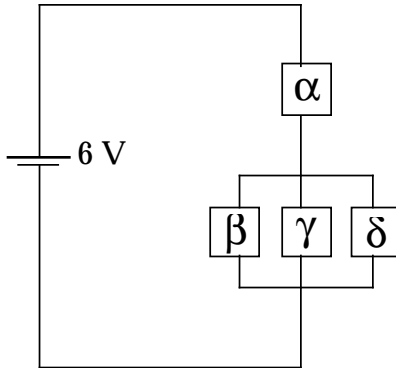


## Circuits with Resistors and Capacitors—Current <sup>163</sup>

The circuit shown below has circuit elements  $\alpha$ ,  $\beta$ ,  $\gamma$ , and  $\delta$ , which are either a 1 F capacitor or a 1, 2, or 4 ohm resistor. Rank the arrangements of circuit elements given below in order from largest to smallest magnitude of current that flows after a long time through the 6 volt battery connected as shown.



Arrangements	$\alpha$	$\beta$	$\gamma$	$\delta$
Arrangement A	1F=1 Farad	$4\Omega = 4$ ohms	$1\Omega = 1$ ohm	$2\Omega = 2$ ohms
Arrangement B	$1\Omega$	1F	$2\Omega$	$4\Omega$
Arrangement C	$2\Omega$	$1\Omega$	$4\Omega$	1F
Arrangement D	$4\Omega$	$2\Omega$	1F	$1\Omega$
Arrangement E	1F	$1\Omega$	$2\Omega$	$4\Omega$
Arrangement F	$1\Omega$	$4\Omega$	$2\Omega$	1F
Arrangement G	$2\Omega$	$4\Omega$	1F	$1\Omega$

Ranking of arrangements by magnitude of current through the battery:

Largest   1\_\_\_\_\_ 2\_\_\_\_\_ 3\_\_\_\_\_ 4\_\_\_\_\_ 5\_\_\_\_\_ 6\_\_\_\_\_ 7\_\_\_\_\_   Smallest

Which of these arrangements have the same magnitude of current, if any?

\_\_\_\_\_

Please carefully explain your reasoning.

How sure were you of your ranking? (circle one)

Basically Guessed

Sure

Very Sure

1      2      3      4      5      6      7      8      9      10

<sup>163</sup> K. Wetz