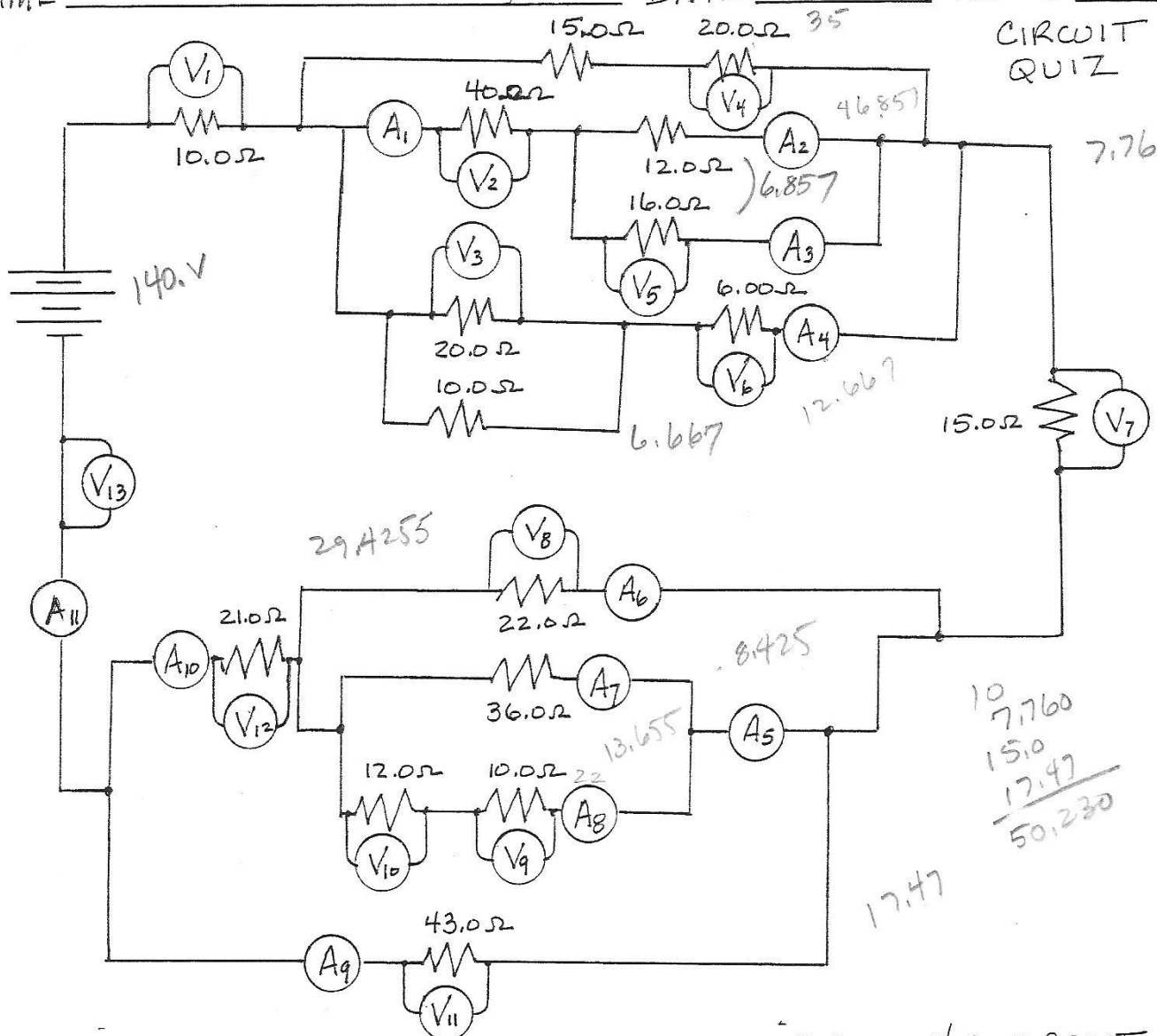


NAME _____

DATE _____

PERIOD _____

CIRCUIT
QUIZ

SOLVE FOR ALL VOLTMETERS AND AMMETERS IN THIS CIRCUIT.

A_1 0.462 A
 A_2 0.264 A
 A_3 0.198 A
 A_4 1.71 A
 A_5 1.02 A
 A_6 0.634 A
 A_7 0.387 A
 A_8 0.634 A
 A_9 1.13 A
 A_{10} 1.65 A
 A_{11} 2.79 A

V_1 27.9 V
 V_2 18.5 V
 V_3 11.4 V
 V_4 12.4 V
 V_5 3.17 V
 V_6 10.2 V
 V_7 41.8 V
 V_8 13.9 V
 V_9 6.34 V
 V_{10} 7.60 V
 V_{11} 48.7 V
 V_{12} 34.7 V
 V_{13} 0 V