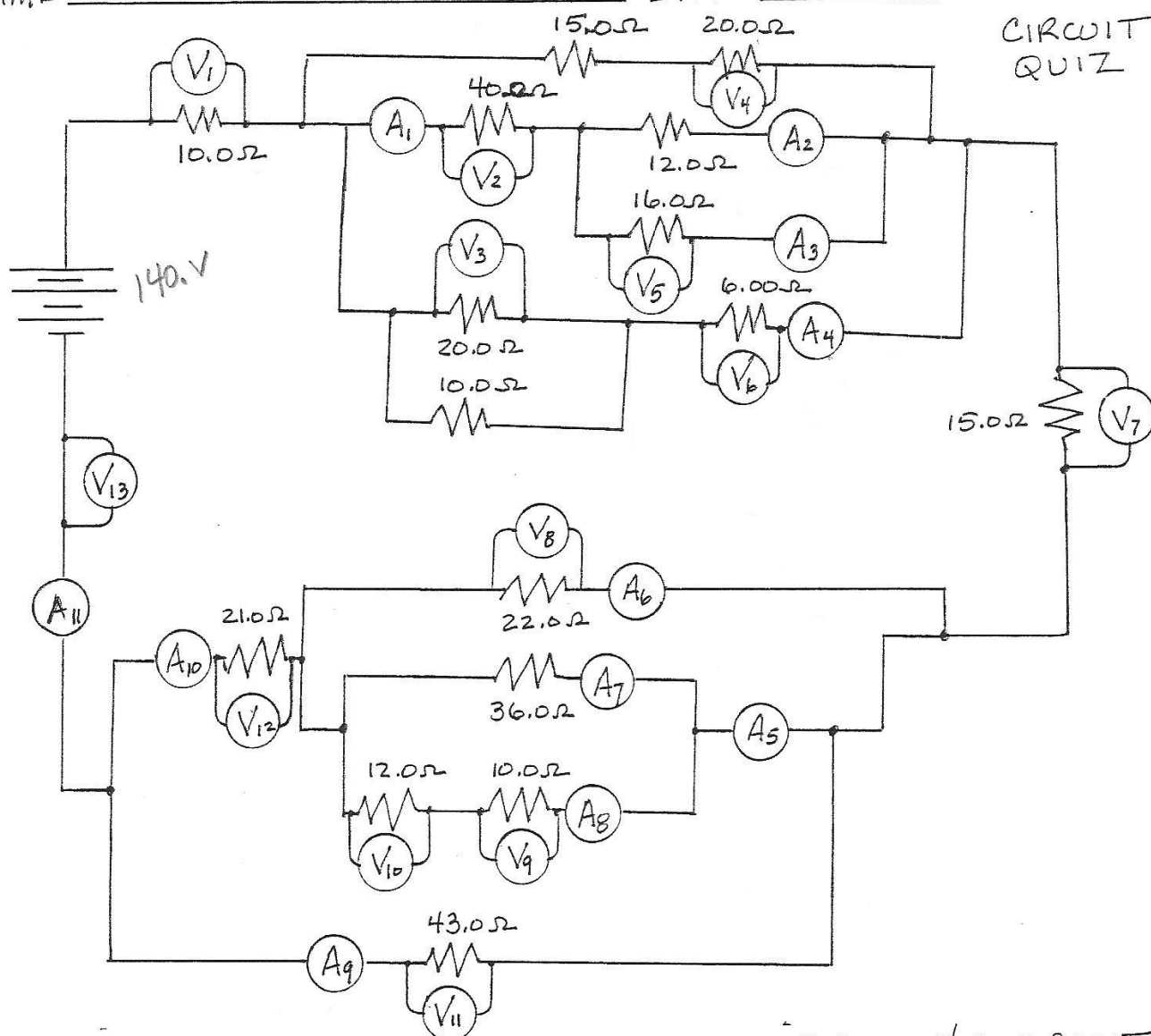


NAME _____

DATE _____

PERIOD _____

CIRCUIT QUIZ



SOLVE FOR ALL VOLTMETERS AND AMMETERS IN THIS CIRCUIT.

A_1 _____
 A_2 _____
 A_3 _____
 A_4 _____
 A_5 _____
 A_6 _____
 A_7 _____
 A_8 _____
 A_9 _____
 A_{10} _____
 A_{11} _____

V_1 _____
 V_2 _____
 V_3 _____
 V_4 _____
 V_5 _____
 V_6 _____
 V_7 _____
 V_8 _____
 V_9 _____
 V_{10} _____
 V_{11} _____
 V_{12} _____
 V_{13} _____